

- CE
- ROHS
- Xilinx
- Digilent Inc.
- Chinese ROHS
- Analog Devices

- F1 Foot
- F2 Foot
- F3 Foot
- F4 Foot





Title		Rev	
<h1>Nexys A7</h1>		<h1>D.2</h1>	
		Copyright 2021	
Circuit	PMOD_I/O	Author	DL
Doc#	500-292	Date	12/23/2021
Engineer	EG	Sheet#	1 out of 11



DIGILENT[®]
A National Instruments Company

Terms of Use. The contents are provided "AS IS". DIGILENT DISCLAIMS ALL WARRANTIES, EITHER EXPRESS OR IMPLIED, INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF INTELLECTUAL PROPERTY. The contents could contain technical inaccuracies, typographical errors or out-of-date information. Information may be updated or changed at any time, without notice. Use of such information is therefore at your own risk. Digilent may at any time revise these Terms of Use. You are bound by such revisions and should therefore visit <https://store.digilentinc.com/terms-of-use/> to review the current Terms of Use.




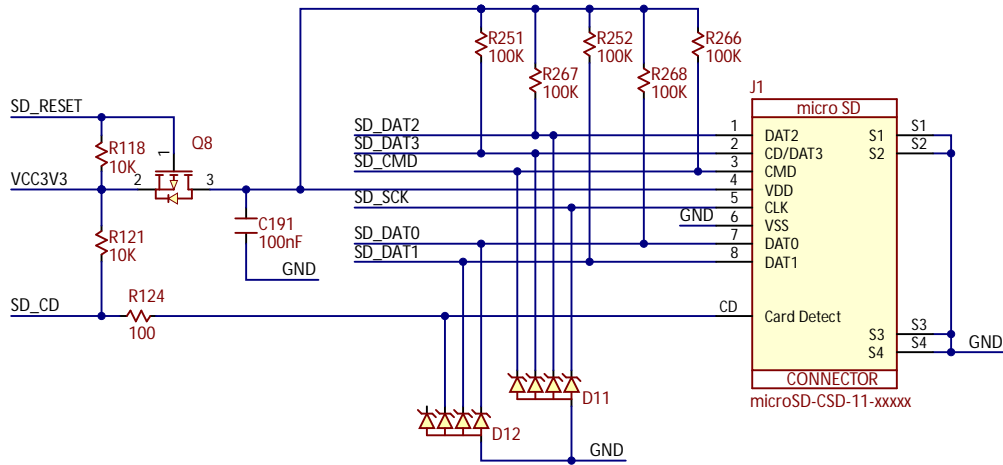
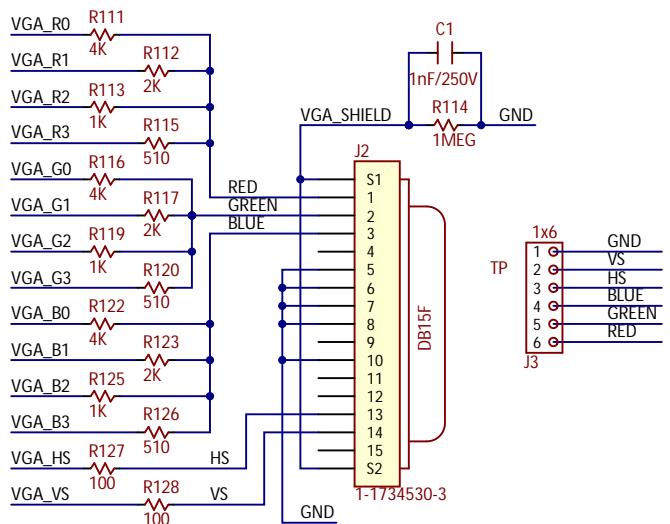
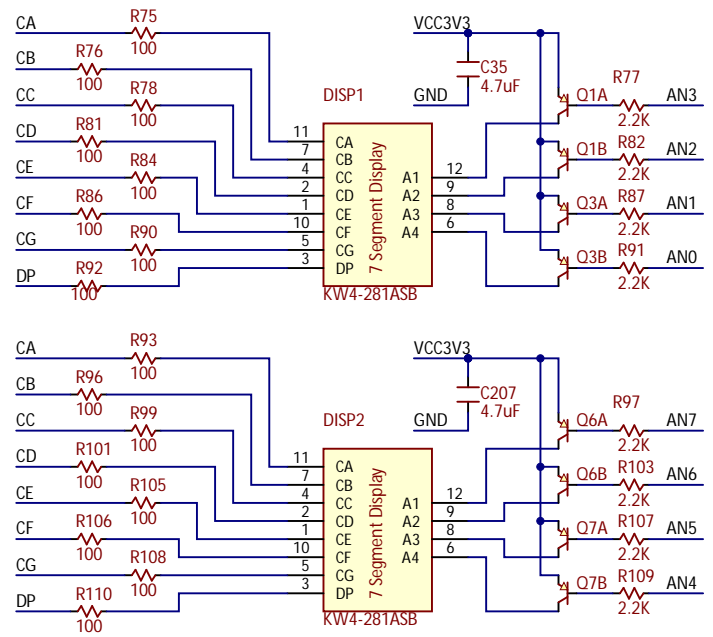
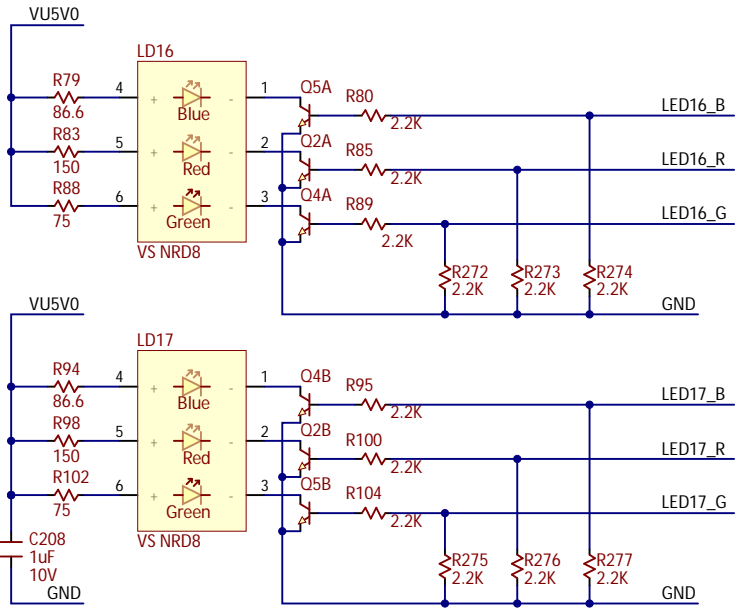
Limitation of Liability. DIGILENT WILL NOT BE LIABLE FOR DIRECT, INDIRECT, SPECIAL, INCIDENTAL, COVER, ECONOMIC, OR CONSEQUENTIAL DAMAGES ARISING OUT OF THE USE OR INABILITY TO USE THE CONTENTS EVEN IF DIGILENT IS ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.



Title		Rev
<h1>Nexys A7</h1>		<h2>D.2</h2>
Circuit		Copyright 2021
7 SEG, VGA, SD		
Doc#	500-292	
Engineer	EG	
Author	DL	
Date	12/23/2021	
Sheet#	2 out of 11	







DIGILENT
A National Instruments Company

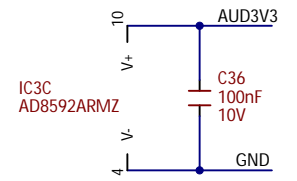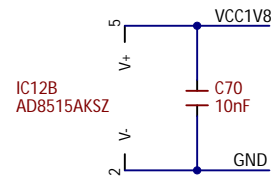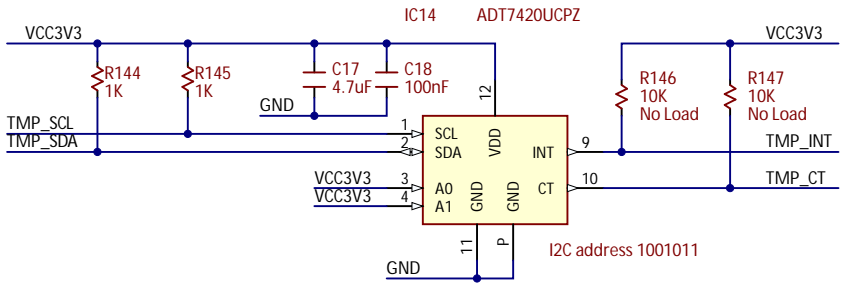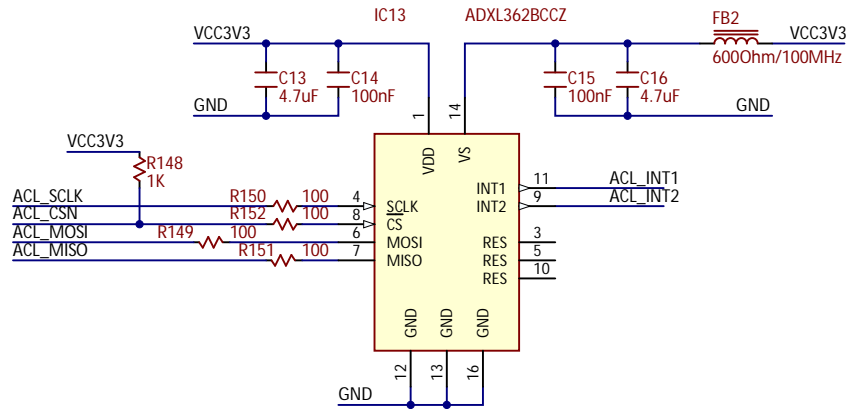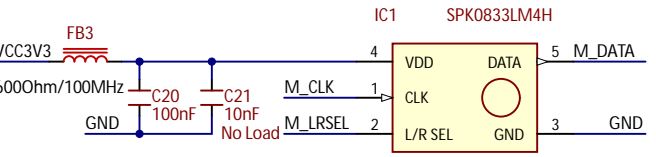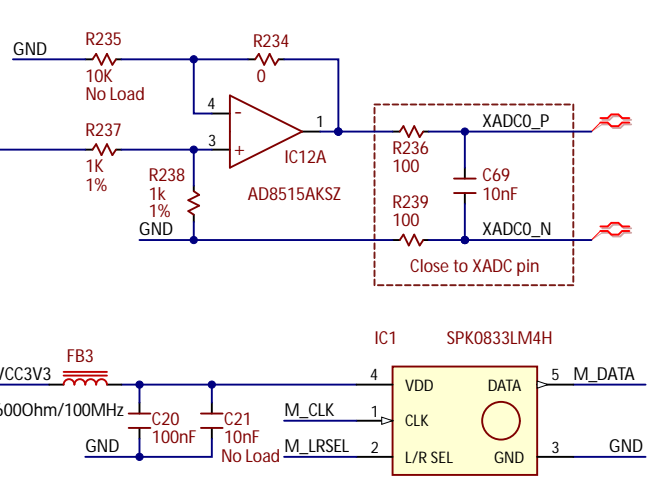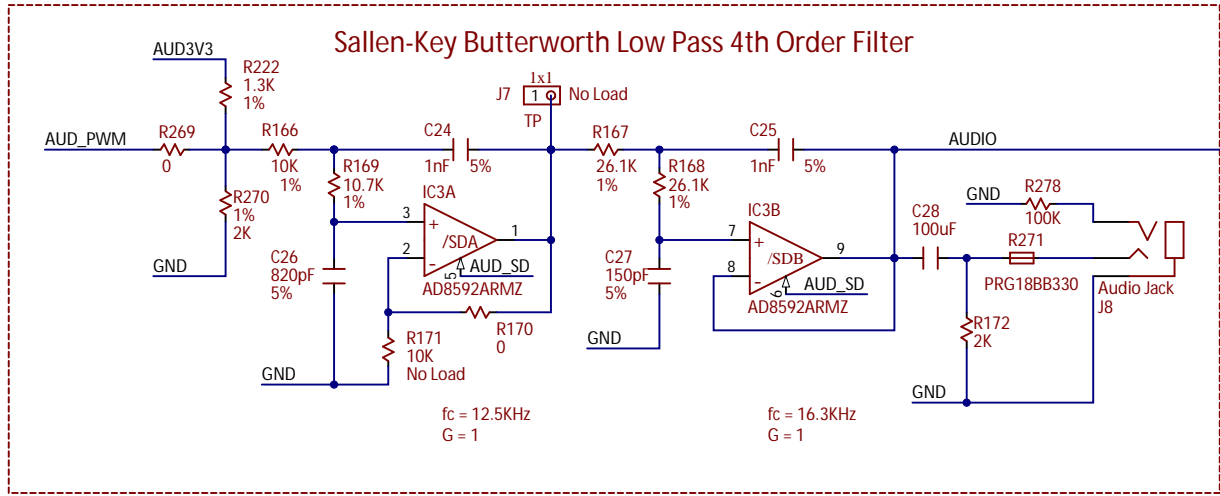


For more information on the parts used in this design, please refer to:

- <http://www.analog.com/ad8592> (CMOS Single Supply RRIO Dual Op Amp with ±250 mA Output Current and Shutdown Mode)
- <http://www.analog.com/ad8515> (1.8 V Low Power CMOS Rail-to-Rail Input/Output Operational Amplifier)
- <http://www.analog.com/adxl362> (Micropower, 3-Axis, ±2 g/±4 g/±8 g Digital Output MEMS Accelerometer)
- <http://www.analog.com/adt7420> (±0.25°C Accurate, 16-Bit Digital I2C Temperature Sensor)

Title <h1 style="margin: 0;">Nexys A7</h1>		Rev <h1 style="margin: 0;">D.2</h1>
Circuit ETH, TMP, ACL_AUDIO		Copyright 2021
Doc# 500-292		 DIGILENT [®] A National Instruments Company
Engineer EG		
Author DL		
Date 12/23/2021		
Sheet# 3 out of 11		

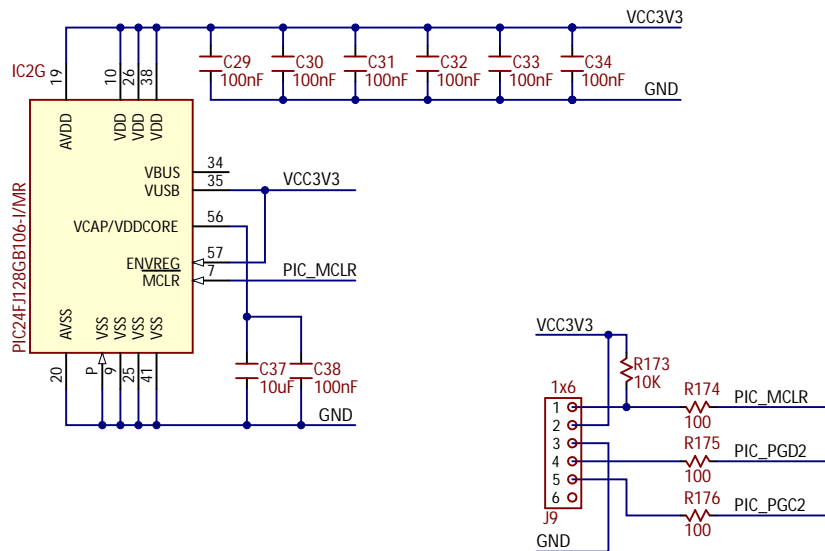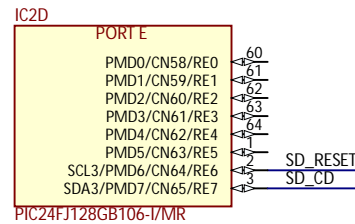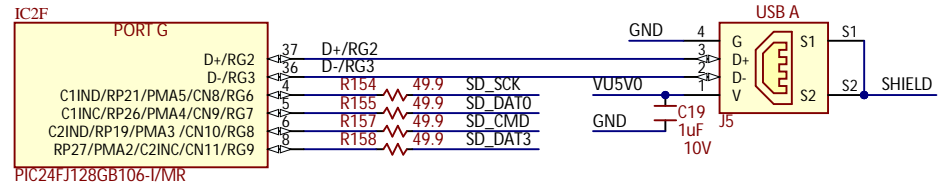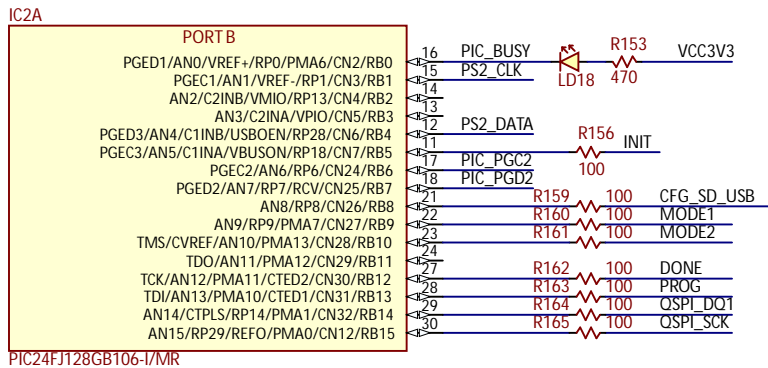

Title		Nexys A7		Rev		D.2	
Circuit		USB HID		Copyright		2021	
Doc#		500-292		 A National Instruments Company			
Engineer		EG					
Author		DL					
Date		12/23/2021					
Sheet#		4 out of 11					

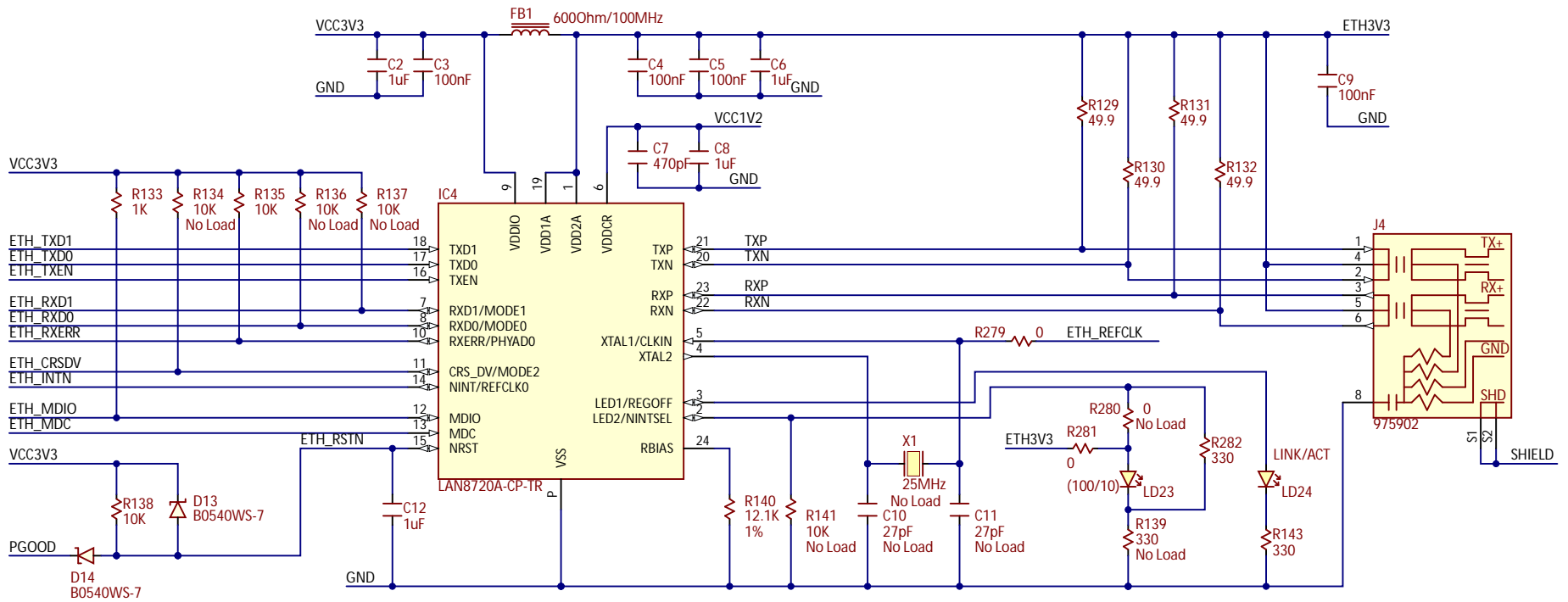

Title		Rev
Nexys A7		D.2
		Copyright 2021
Circuit	ETHERNET	
Doc#	500-292	
Engineer	EG	
Author	DL	
Date	12/23/2021	
Sheet#	5 out of 11	



This Page Intentionally Left Blank

Title		Rev
Nexys A7		D.2
		Copyright 2021
Circuit	USB PROG/UART	
Doc#	500-292	
Engineer	EG	
Author	DL	
Date	12/23/2021	
Sheet#	6 out of 11	



For the -50T variant: IC8=XC7A50T-1CSG324I

IC8B





IC8D

IC8E

BANK 15







BANK 34

BANK 35

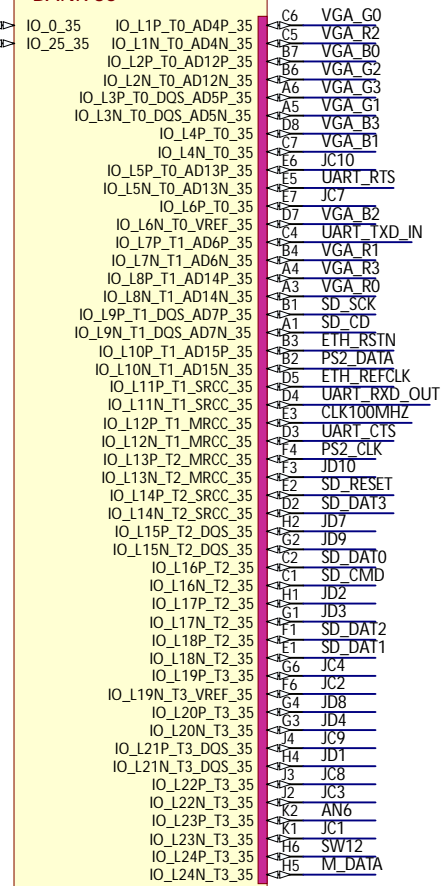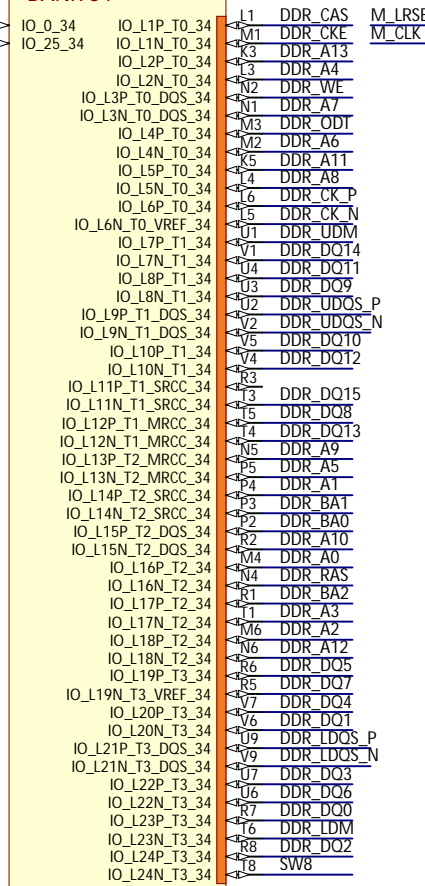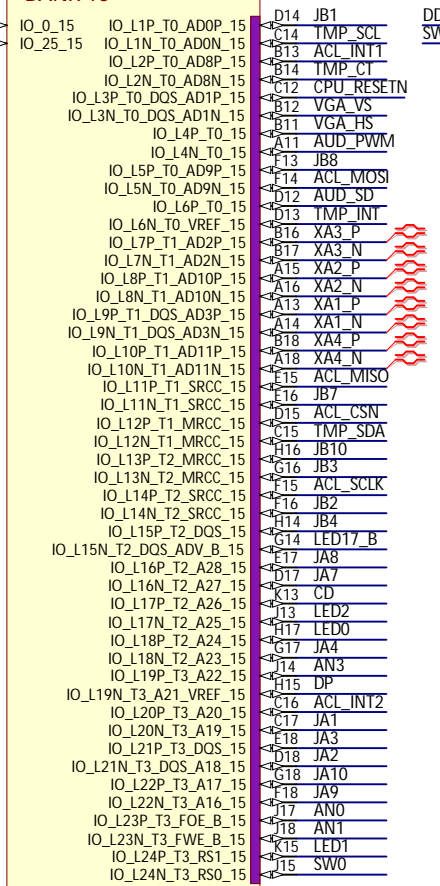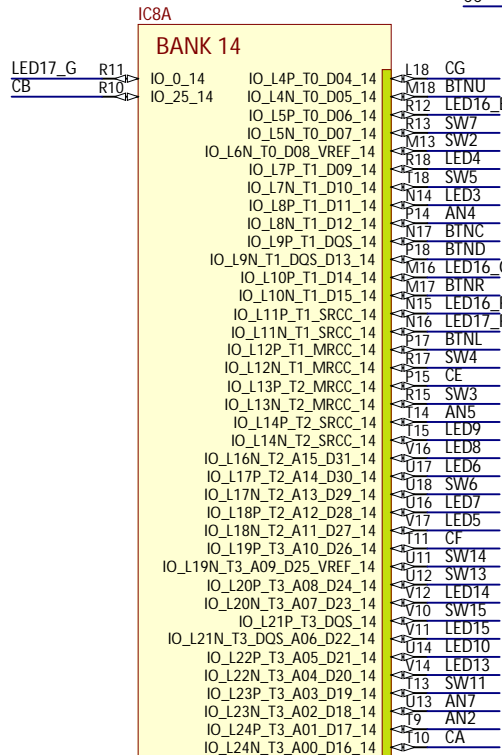

IC8C


IC8C

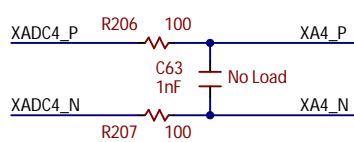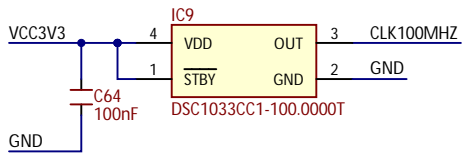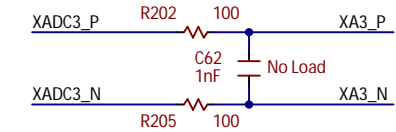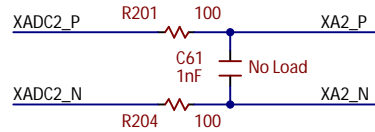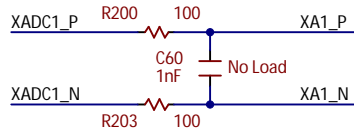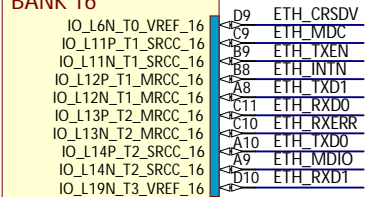

Title	Nexys A7		Rev	D.2
Circuit	FPGA BANKS		Copyright 2021	
Doc#	500-292			
Engineer	EG			
Author	DL			
Date	12/23/2021			
Sheet#	7 out of 11			



A National Instruments Company

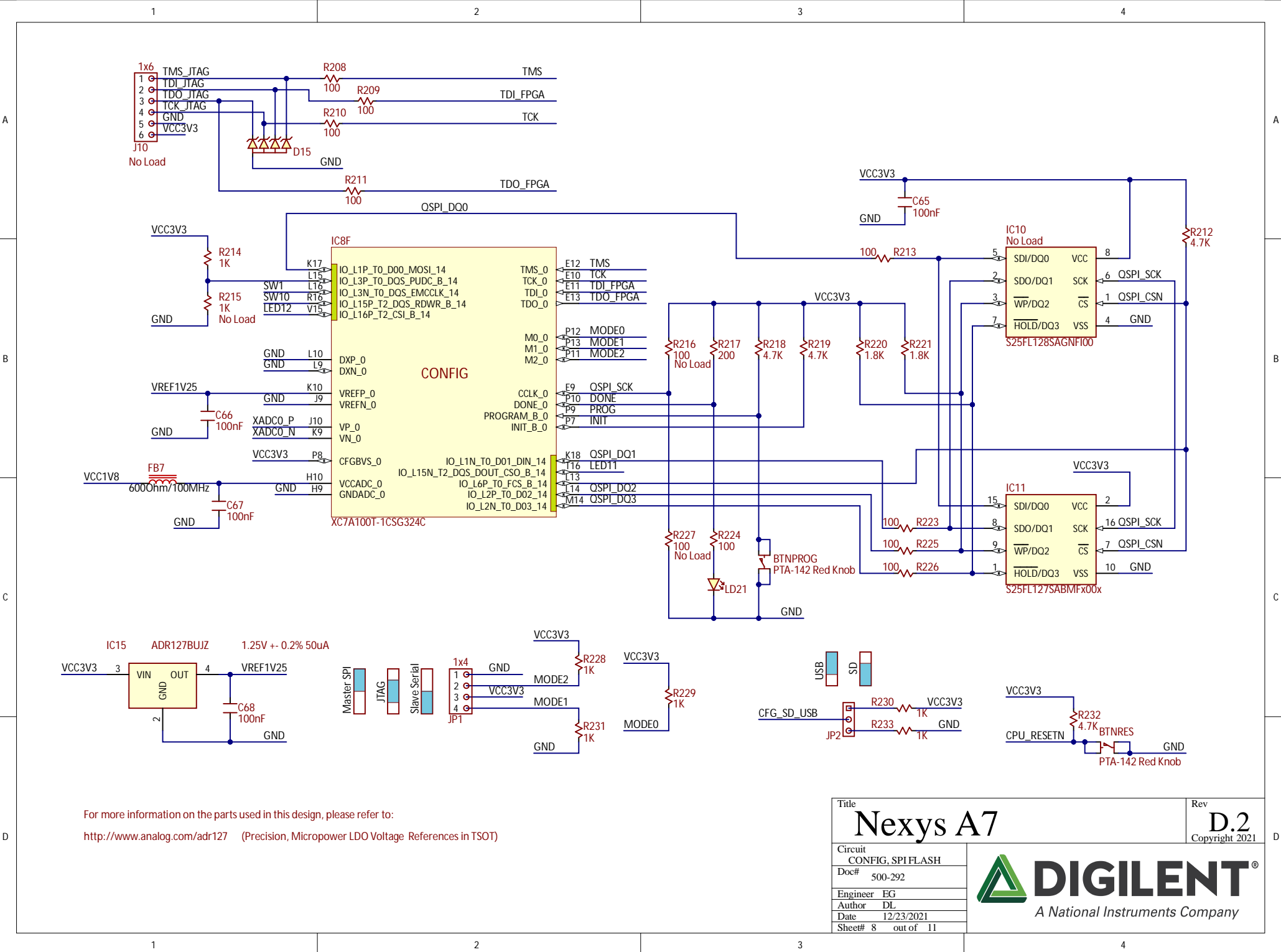


For more information on the parts used in this design, please refer to:
<http://www.analog.com/adr127> (Precision, Micropower LDO Voltage References in TSOT)

Title		Rev
<h1>Nexys A7</h1>		<h2>D.2</h2>
Circuit		Copyright 2021
CONFIG, SPIFLASH		
Doc#	500-292	
Engineer	EG	
Author	DL	
Date	12/23/2021	
Sheet#	8 out of 11	







DIGILENT
A National Instruments Company

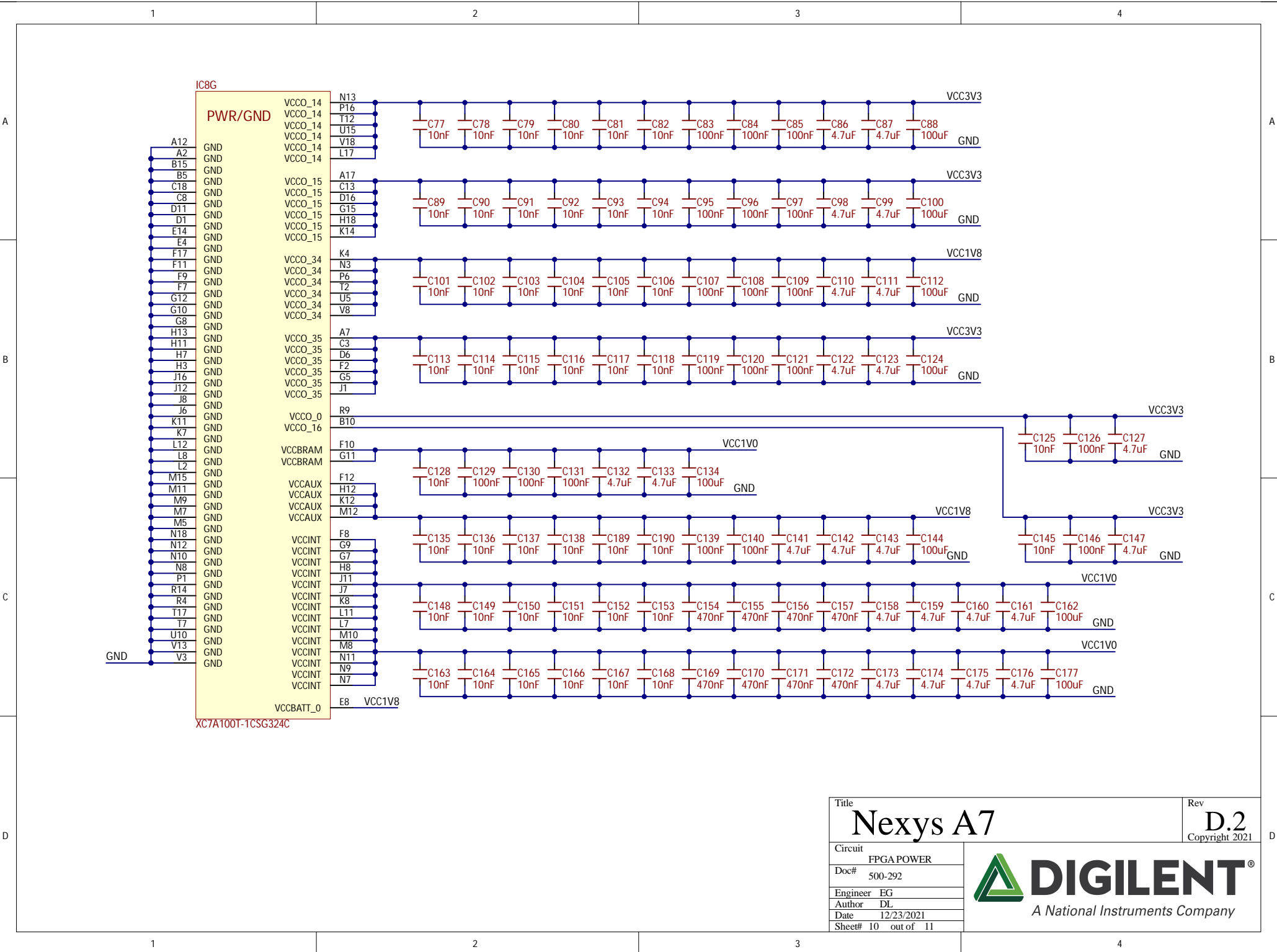

Title		Rev
<h1>Nexys A7</h1>		<h2>D.2</h2>
		Copyright 2021
Circuit	FPGA POWER	
Doc#	500-292	
Engineer	EG	
Author	DL	
Date	12/23/2021	
Sheet#	10 out of 11	



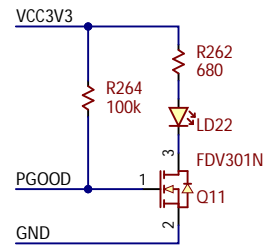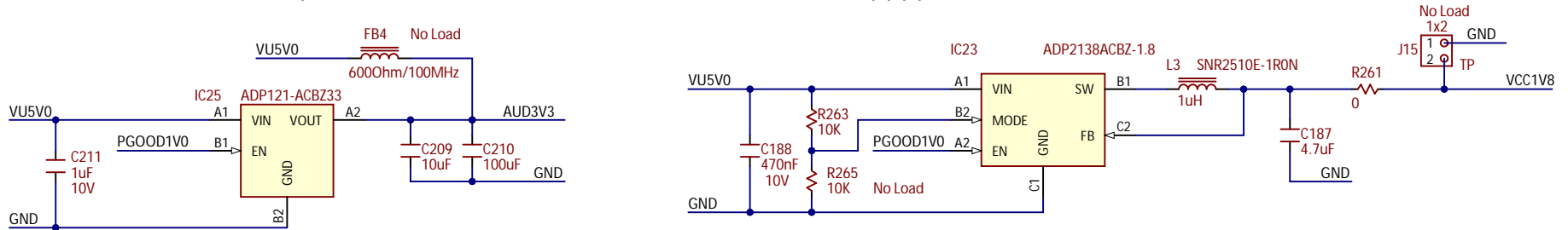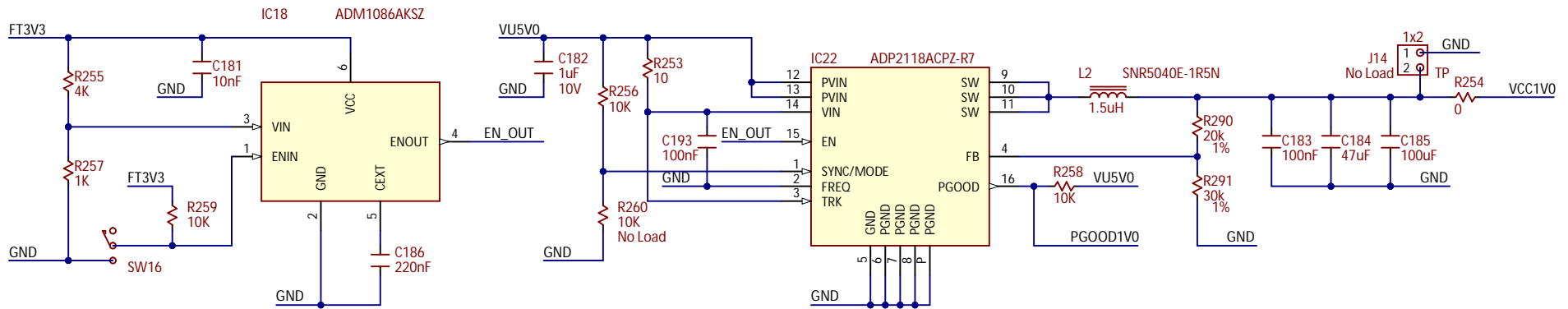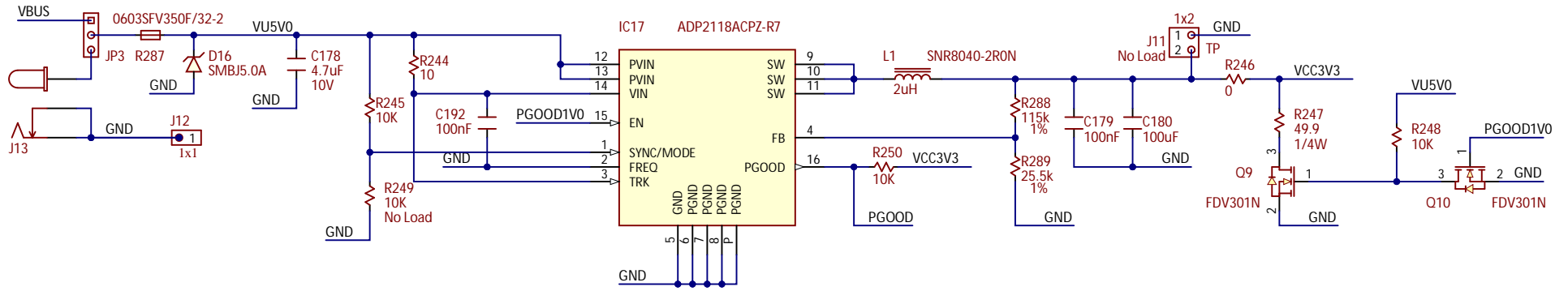DIGILENT[®]
A National Instruments Company



For more information on the parts used in this design, please refer to:

- <http://www.analog.com/adp2118> (3 A, 1.2 MHz/600 kHz High Efficiency Synchronous Step-Down DC-to-DC Regulator)
- <http://www.analog.com/adm1086> (Voltage Sequencer with Active High, Push-Pull Enable Output)
- <http://www.analog.com/adp2138> (Compact, 800 mA, 3 MHz, Step-Down DC-to-DC Converter)
- <http://www.analog.com/adp2121> (CMOS Linear Regulator, 150 mA, Low Quiescent Current)

Title		Rev
<h1>Nexys A7</h1>		D.2
		Copyright 2021
Circuit	POWER	
Doc#	500-292	
Engineer	EG	
Author	DL	
Date	12/23/2021	
Sheet#	11 out of 11	



A National Instruments Company